

LAB 11: AC-DC Power Supply Design

Contents


Executive Summary.....	3
Objective.....	3
AC-DC Stage 1, Filter (LAB).....	3
AC-DC Stage 2, Filter, Zener (LAB).....	5
AC-DC Stage 2, Filter, Zener (LAB).....	5
AC-DC Stage 3, Filter, Zener, BJT (LAB).....	5
AC-DC Stage 1, Transformer (SIM).....	5
AC-DC Stage 1.5, Transformer/GND (SIM).....	5
AC-DC Stage 2, Bridge Rectifier (SIM).....	5
AC-DC Stage 3, Filter (SIM).....	5
AC-DC Stage 4, Filter, Zener (SIM).....	5
AC-DC Stage 5, Filter, Zener, BJT (SIM).....	5
Analysis.....	9
Addendum or Reference.....	8
Excel Generated Data.....	9

configurations were analyzed, with the value of the ripple voltage decreasing steadily with each circuit configuration. In the lab portion, transformer only configuration had the greatest peak to peak value at 19Vpp, resembling that of the input AC wave, while the filter, Zener, and BJT configuration was able to successfully reduce the Vripple down the most, to 4.9mV, with simulations of the same circuits providing similar results.


AC-DC Stage 1, Filter (LAB)

The circuit diagram shows an AC voltage source V_1 with parameters $V_{OFF} = 0$, $V_{AMPL} = 166V$, $FREQ = 60$, and $AC =$. The source is connected to a resistor $R1$ (0.1) in series with an inductor $L1$ (10mH). The output terminals are labeled V_{p+} and V_{p-} . The circuit is coupled to a full-bridge rectifier consisting of four diodes $D1, D2, D3, D4$. The input to the bridge is V_{in_plus} and V_{in_minus} . The bridge output is connected to a filter capacitor $C1$ (1m) and a load resistor $R2$ (50). The output voltage is V_{filt} . The coupling factor is $K1$ (K_Linear) with $COUPLING = 0.14$.

PSpice Generated Plots

 

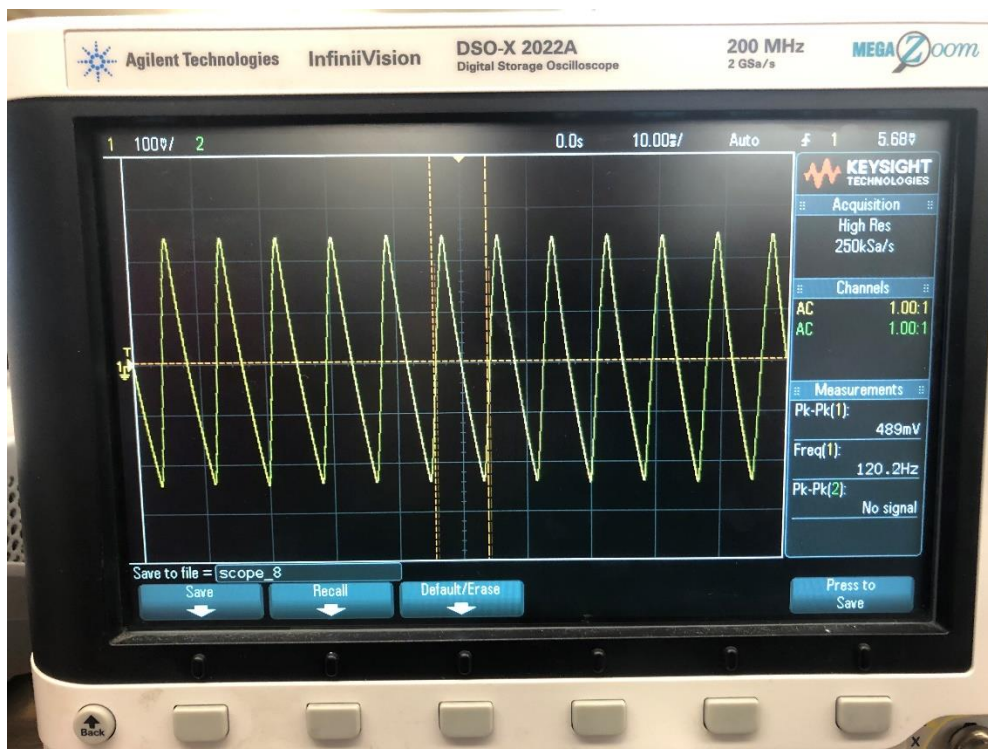
Picture of $V_{in+}/V_{in-} = 19V_{pp}$, the voltage after the center tap transformer has been applied.




$V_{filt}=489mV_{pp}$, the waveform is currently unregulated, but the capacitor's discharge and charge behavior allow the input voltage ($19V_{pp}$) to constantly refresh to its peak as determined by the time constant $T=RC$. For this simulation we used $C=1mF$, $R=50\Omega$, $T=50*1(10^{-3})=0.05s$ or $50ms$. Period is $T=1/f=1/120=0.0083\approx 10ms$. So, whereas the voltage would decay to 0 in about 4 time constants time ($200ms$), it is instead refreshed every $10ms$. The capacitor decay rate is $V(t)=V_i(e^{-(t/RC)})$.

AC-DC Stage 2, Filter, Zener (LAB)

Schematic

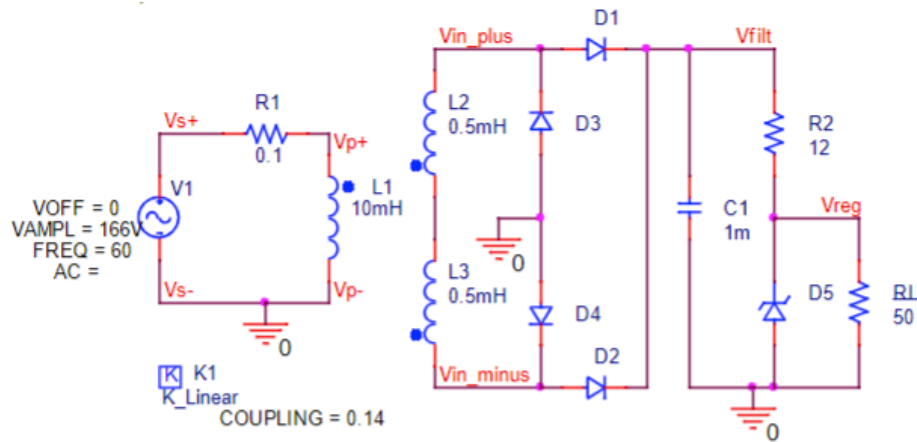


PSpice Generated Plots

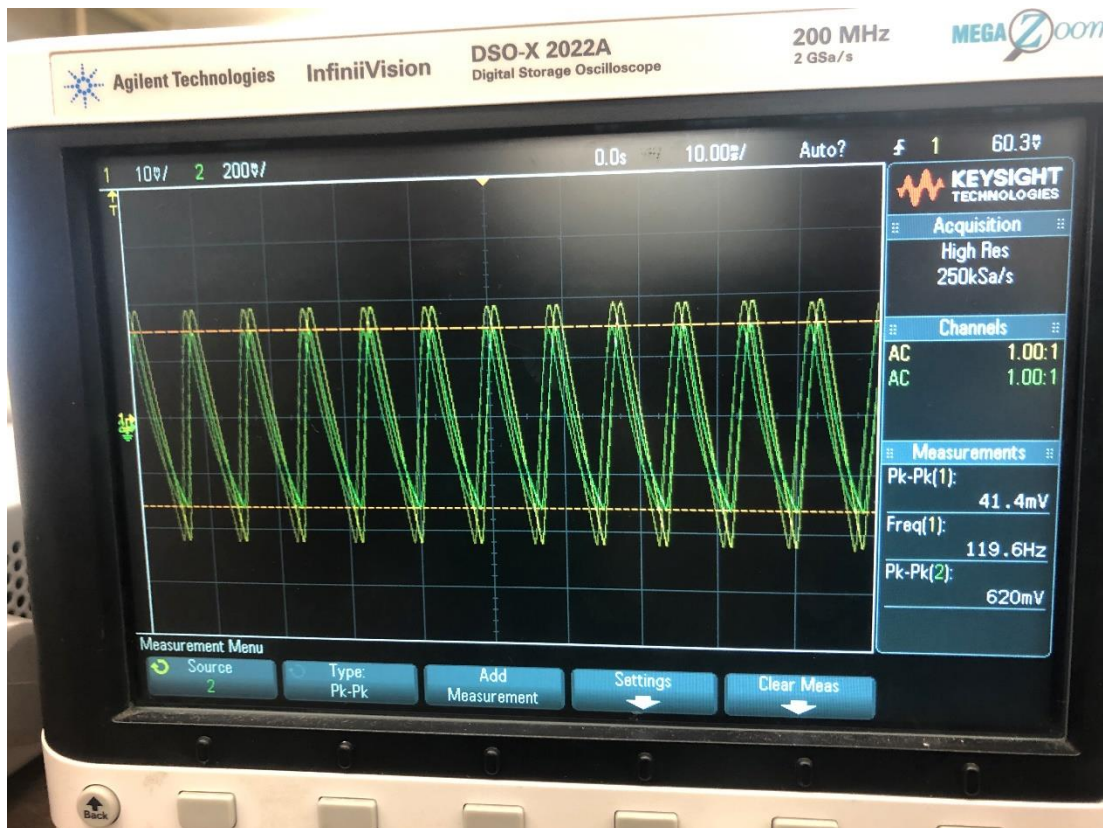


Note that the picture is a bit blurry, but the correct waveform is shown. The 120Hz frequency and 620mVpp of the Vreg is shown alongside the 41.4mVpp of Vfilt, the voltage before Zener regulation.

AC-DC Stage 3, Filter, Zener, BJT (LAB)

Schematic

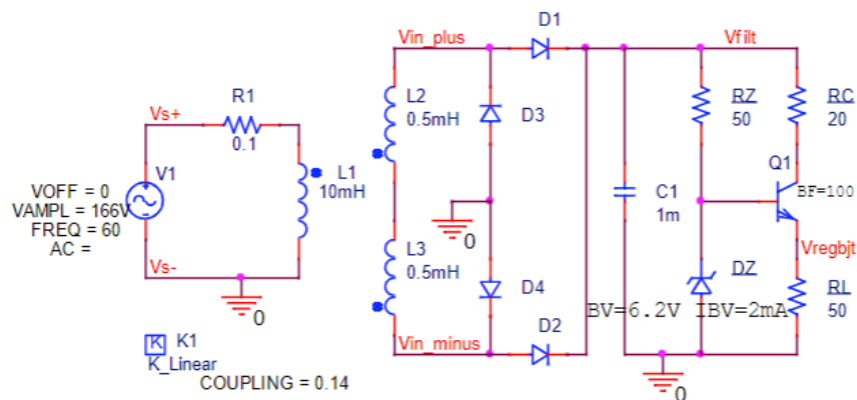


PSpice Generated Plots

 

Fully regulated voltage V_{regbjt} is much lower than the V_{reg} of the filter & zener only (Stage 2) configuration. The 50 ohm resistor ensures that I_b is small compared to I_c , which has a 20 ohm resistor. The small I_b is also I_z flowing into the Zener diode, and because of the V regulation of the Zener, we are placed further UP the Zener breakdown voltage line in the negative x axis. Therefore, there is less variance or ripple in our V_z when compared to the stage 2 configuration.

AC-DC Stage 1, Transformer (SIM)


Schematic

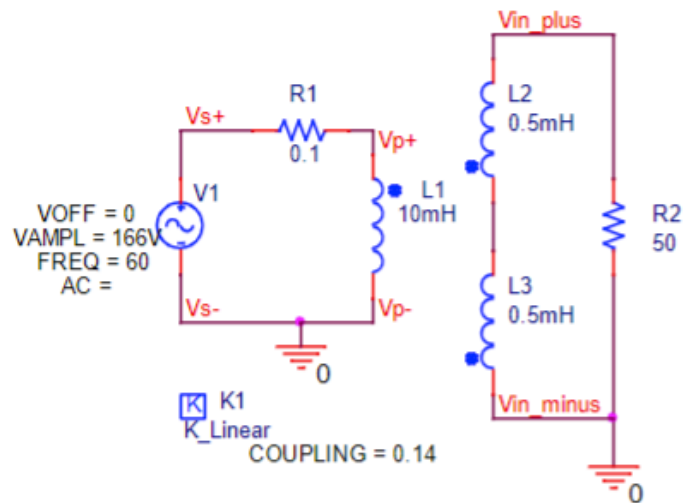

Simulation Profile

General	Analysis	Configuration Files	Options	Data Collection	Probe Window
Analysis Type: Time Domain (Transient)					
Options: <div style="display: flex; justify-content: space-between;"> <div> <input checked="" type="checkbox"/> General Settings <input type="checkbox"/> Monte Carlo/Worst Case <input type="checkbox"/> Parametric Sweep <input type="checkbox"/> Temperature (Sweep) <input type="checkbox"/> Save Bias Point <input type="checkbox"/> Load Bias Point <input type="checkbox"/> Save Check Point <input type="checkbox"/> Restart Simulation </div> <div> Run To Time : 500ms seconds (TSTOP) Start saving data after : 400ms seconds Transient options: Maximum Step Size: 0.5m seconds <input type="checkbox"/> Skip initial transient bias point calculation (SKIPBP) <input type="checkbox"/> Run in resume mode </div> <div> Output File Options... </div> </div>					
<div> OK Cancel Apply Reset Help </div>					


Excel Generated Plots

 

The transformer successfully converts the large 166Vp AC input voltage to ~6Vp.

AC-DC Stage 1.5, Transformer/GND (SIM)

Schematic

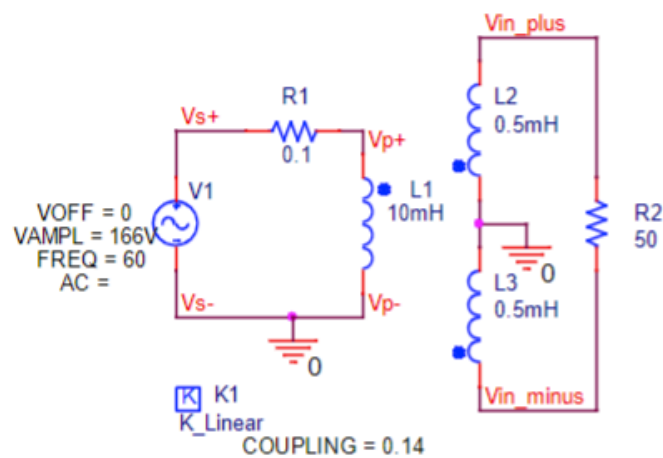

Simulation Profile

General Analysis Configuration Files Options Data Collection Probe Window

Analysis Type: Time Domain (Transient)

Options:

- ☒ General Settings
- ☐ Monte Carlo/Worst Case
- ☐ Parametric Sweep
- ☐ Temperature (Sweep)
- ☐ Save Bias Point
- ☐ Load Bias Point
- ☐ Save Check Point
- ☐ Restart Simulation

Run To Time : 500ms seconds (TSTOP)

Start saving data after : 400ms seconds

Transient options:

Maximum Step Size 0.5m seconds


☐ Skip initial transient bias point calculation (SKIPBP)

☐ Run in resume mode

Output File Options...

OK Cancel Apply Reset Help


Excel Generated Plots

 


Vinplus and Vinminus swings between the max and min values of the rectified output voltage, 180 degrees out of phase.

AC-DC Stage 2, Bridge Rectifier (SIM)

Schematic

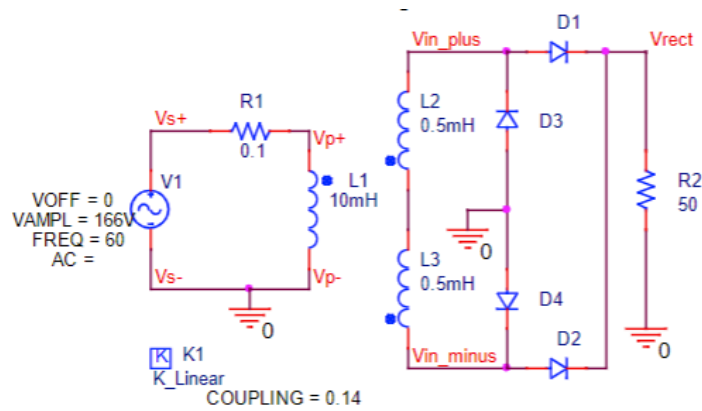


Excel Generated Plots

 


With the rectifier in place, the Vinminus portion of the input voltage at the transformer is flipped to positive, meaning that the frequency has now been doubled from 60Hz to 120Hz. Vrect at the resistor is slightly lower because of the diode activation voltages.

AC-DC Stage 3, Filter (SIM)

Schematic

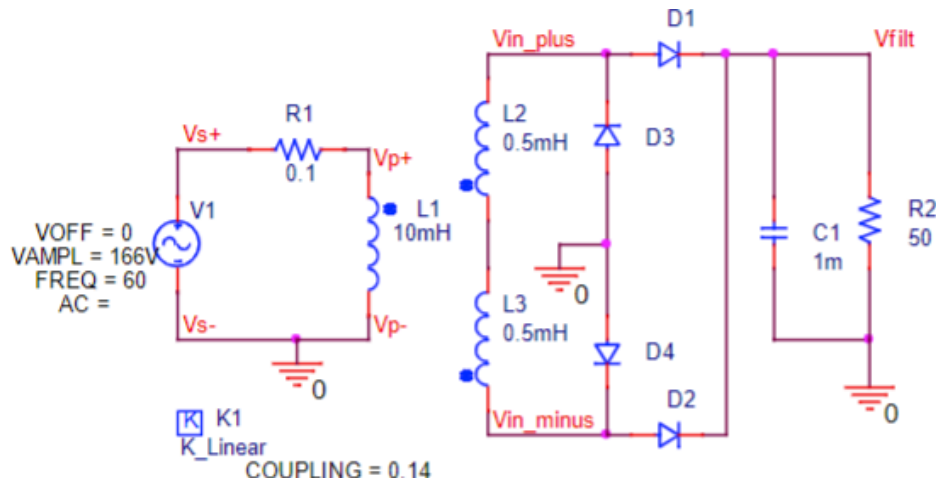


Excel Generated Plots

 


Comparing this plot to the load resistor configuration plot, we notice that the top of the Vrect waveform has been isolated and the new Vfilt signal is now slightly out of phase to the input signal due to the capacitor's discharge time. There are voltage fluctuations @ the input Vinplus and Vinminus around the time when the capacitor discharges and refreshes the voltage @ Vrect. This likely occurs at the input voltage before the capacitor in the circuit because some voltage is being drained by the capacitor for charging. Note the ripple voltage is $\sim 0.4V_p$. RRR is about $20\log_{10}(8.63/9.33) = -0.677$.


AC-DC Stage 4, Filter, Zener (SIM)

Schematic

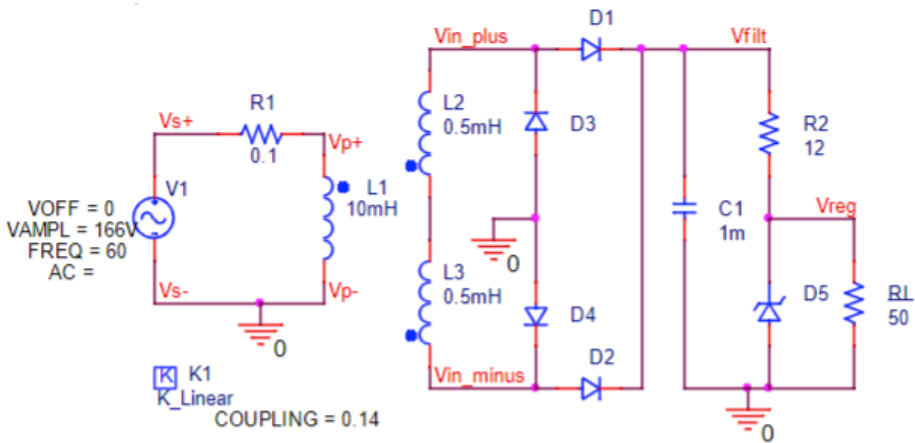

Excel Generated Plots

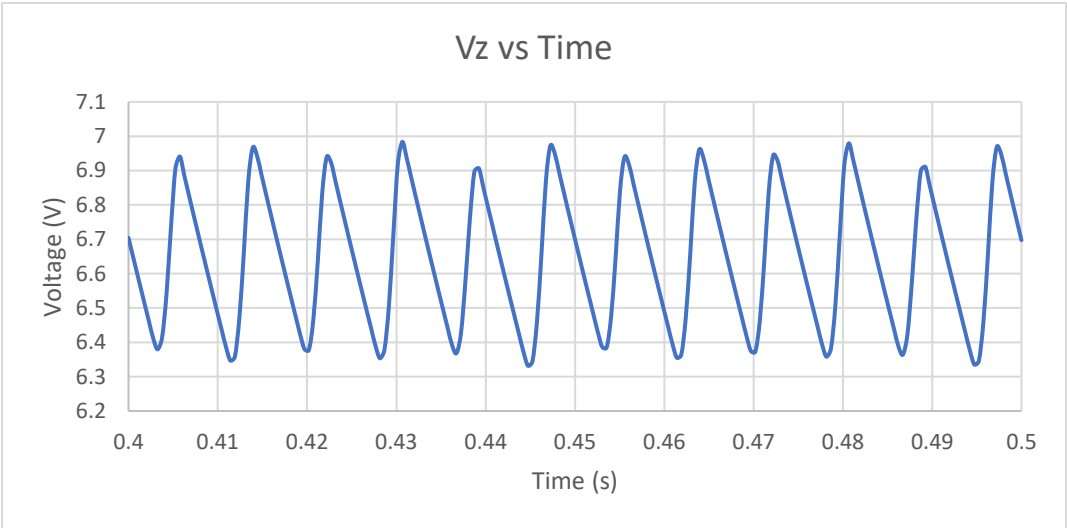

 


For plot 1, the Zener diode's breakdown voltage fluctuates from ~6.7V with fluctuations of ~0.2V. These fluctuations should be lessened by adding the BJT in the next stage.



For plot 2, the Zener diode regulates the previously 8V Vfilt we see from stage 3, to ~6.2V with a ripple of ~0.1Vp. RRR is about $20\log_{10}(6.7/8.2)=-1.75$.

AC-DC Stage 5, Filter, Zener, BJT (SIM)

Schematic

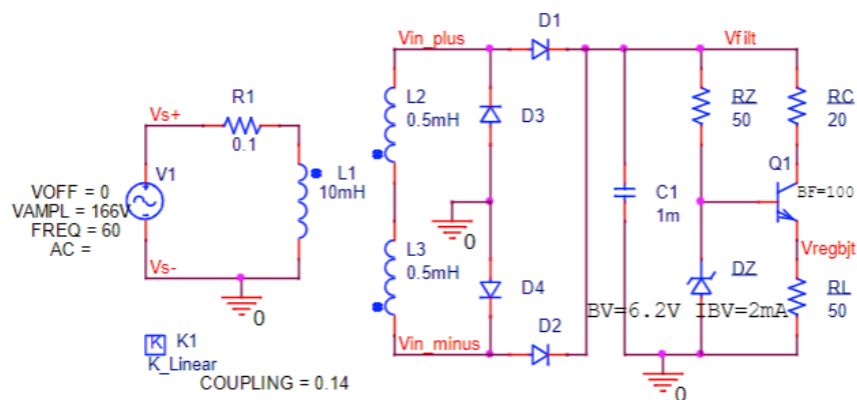

Excel Generated Plots

  

For plot 1, the BJT has effectively reduced the voltage ripple to $\sim 0.06V_p$, much less than the $0.2V_p$ found in the Zener only circuit. Again, this is a result of the resistor configurations lowering the I_z (I_b). On the Zener characteristic curve, lowering the current will create a lower V_z in the breakdown region.

For plot 2, we see that V_{filt} is now 6V as opposed to 8V as a portion of the current as been drawn away from the collector line (where V_{filt} is) into the base line of the transistor. Then the

Zener diode regulates it down to 5V and it is reduced even further at the load by the 50 ohm resistor. ($I_c = I_e$, but $R_c < R_L$). RRR is about $20\log_{10}(4.306/5.517) = -2.15$.

Analysis

Analyzing the final circuit we can trace the behavior of the ripple voltage as each component is applied. First the transformer is used to step down the input 120Vrms AC voltage to an $\sim 20V_{pp}$ AC voltage. The rectifier converts the negative portion of the sine wave to positive, doubling the frequency to 120Hz and creating a V_{rect} that somewhat resembles DC. The capacitor filter prevents the decay of the ripple voltage by discharging during decay and recharging the V_{filt} output voltage. The rate of discharge can be manipulated via capacitance and resistor; it is controlled by the time constant $T = RC$ and dictated by $V(t) = V_i(e^{-t/RC})$. We can now measure the ripple voltage @ V_{filt} to be $\sim 0.4V_p$. The Zener diode acts as the voltage regulator, but drops the output voltage due to its diode activation voltage. Yet it is still not optimized because the higher current I_z results in a higher V_z , which is our V_{reg} . We must use a BJT and a separate resistor to control the current coming into the Zener, splitting it along the base and collector lines so that we are placed further up the Zener breakdown voltage line in the Zener characteristic, reducing our output voltage's ripple even further. Note the RRR differences are from -0.677 w/ the filter only to -2.15 with the filter, Zener, BJT configuration. The values are small because it is a simulation environment, but greater negative values corresponds to a better rejection of the input's ripple at the output (aka less ripple at the output), which corresponds to our findings.

Addendum or Reference

Excel Generated Data (some datasets may be linked if too large)

Simulation Data (Stages 1 to 5)

[2200L-L11sim1.xlsx](#)

[L11sim1.5.xlsx](#)

[L11sim2.xlsx](#)

[L11sim3.xlsx](#)

[L11sim4.xlsx](#)

[L11sim5.xlsx](#)